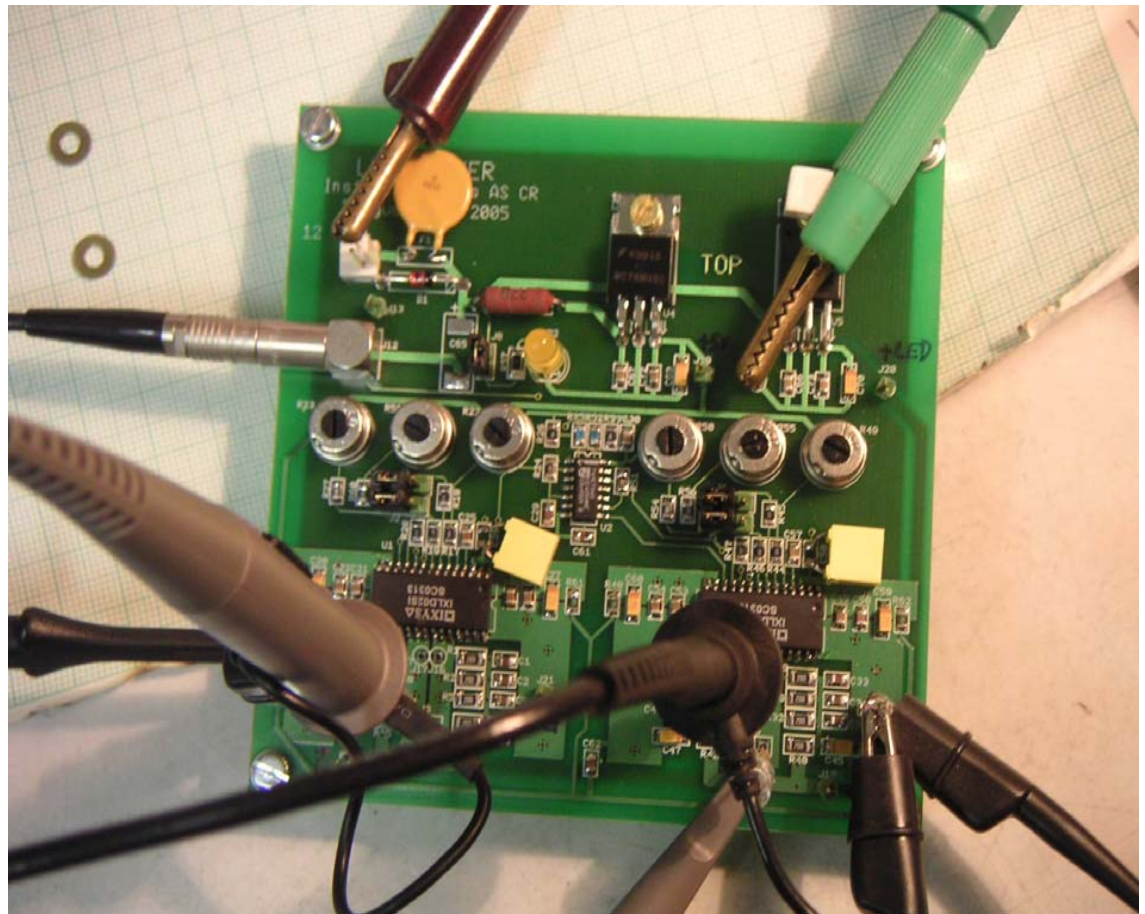


CMB - LED driver

A New 2CH version in focus.


Latest version of 2CH LED driver

- Common input for signal LED-trigger, lemo, 50 Ω
- One 12V (60mA) supply, protection
- Rise time 2ns, tested with P5050 scope probe (8pF, 500MHz)
C=8pF, L=30nH
fres=290MHz



Output, one LED leg, 500MHz passive probe

this is a true RF technique :)

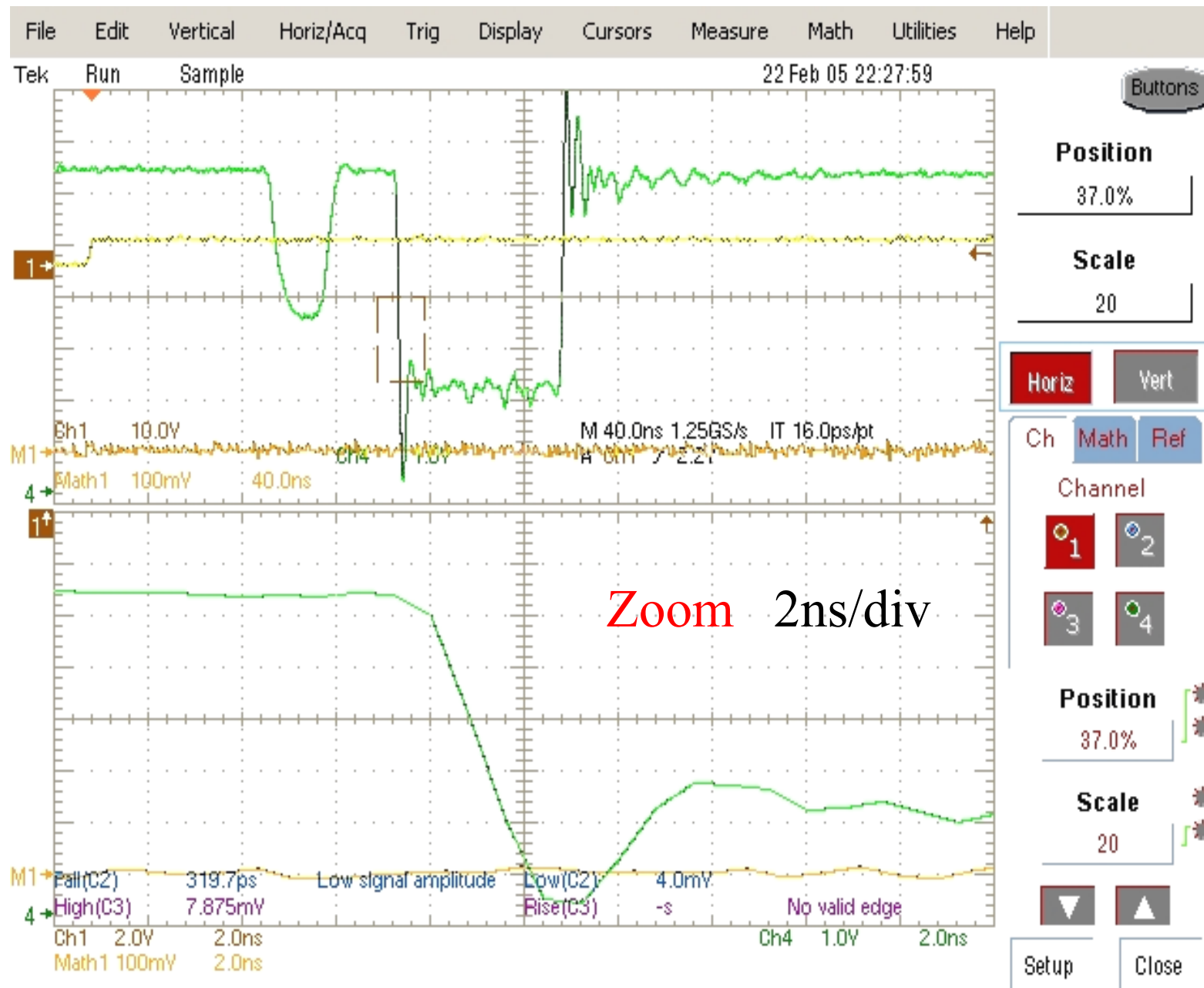

Task for next week

- **LED driver**
 - To optimise a range of puls width (min to 40ns)
 - Test of the current linearity (input vs. output)
- **PINphoto diode** signal chain
 - Define the preamp gain
 - Optimise the BandWidth